

VLSI - FINAL PROJECT REPORT

MANAN CHICHRA - 2022102058

1) Verilog Component

I) ADDER- SUBTRACTOR SUB CIRCUIT

```
adder_sub.v
1  module Adder_Sub(a,b,cin,M,sum,cout);
2  input [3:0]a,b;
3  input cin,M;
4  output wire [3:0]sum;
5  output cout;
6  FullAdd_SUB F1(a[0],b[0],cin,M,sum[0],cout1);
7  FullAdd_SUB F2(a[1],b[1],cout1,M,sum[1],cout2);
8  FullAdd_SUB F3(a[2],b[2],cout2,M,sum[2],cout3);
9  FullAdd_SUB F4(a[3],b[3],cout3,M,sum[3],cout);
10 endmodule
11
12 module FullAdd_SUB(a,b,cin,M,sum,cout);
13 input a,b,cin,M;
14 output wire sum,cout;
15 wire s_M;
16 wire s1,c1,c2,c3;
17 xor(b_M,M,b);
18 xor(s1,a,b_M);
19 xor(sum,s1,cin);
20 and(c1,a,b_M);
21 and(c2,s1,cin);
22 //and(c3,a,cin);
23 or(cout,c1,c2);
24 endmodule
```

In this Adder_Sub module, I have used another module which adds 3 bits – a,b and cin. I have used this submodule four times inside my main module.

The subtraction of unsigned binary numbers can be done most conveniently by means of complements


- Remember that the subtraction $A - B$ can be done by taking the 2's complement of B and adding it to A
- The 2's complement can be obtained by taking the 1's complement and adding 1 to the least significant pair of bits
- The 1's complement can be implemented with inverters, and a 1 can be added to the sum through the input carry
- The circuit for subtracting $A - B$ consists of an adder with inverters placed between

each data input B and the corresponding input of the full adder

- The input carry C_0 must be equal to 1 when subtraction is performed
- The operation thus performed becomes A, plus the 1's complement of B, plus 1.

This is equal to A plus the 2's complement of B

Circuit Reference

 


M = 1 for subtraction

M = 0 for addition

- The mode input M controls the operation
- When M = 0, the circuit is an adder, and when M = 1, the circuit becomes a subtractor
- When M = 0, the full adders receive the value of B, the input carry is 0, and the circuit performs A + B
- When M = 1, the full adders receive B' and C₀ = 1
- Thus, the B inputs are all complemented and a 1 is added through the input carry
- The circuit performs the operation A plus the 2's

complement of B

FA block:

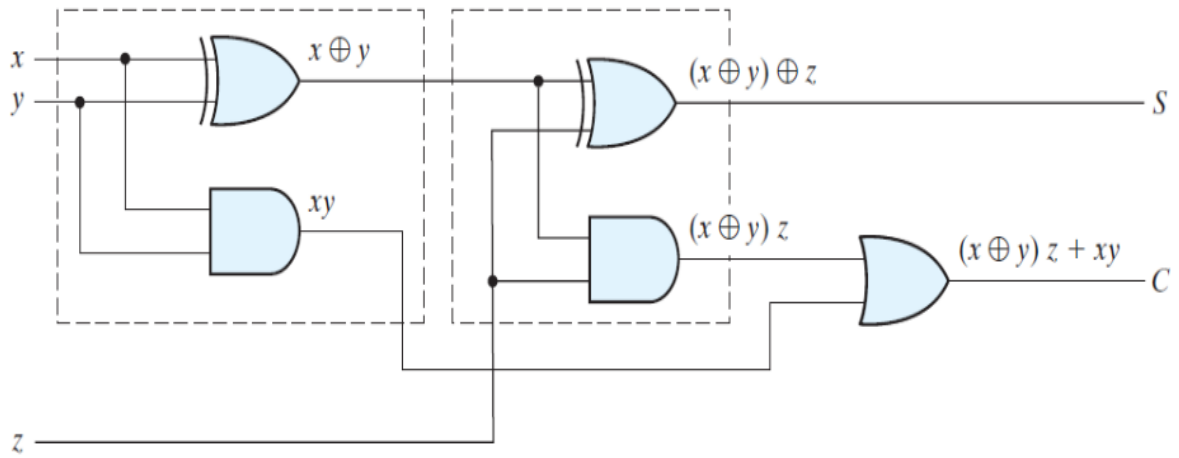

II) COMPARATOR SUB-CIRCUIT

```
comparator.v
1  module bit_comparator (
2      input [3:0] A,
3      input [3:0] B,
4      output equal,
5      output A_greater,
6      output B_greater
7  );
8      wire w0,w1,w2,w3,s0,s1,s2,s3,s4,s5,s6,s7;
9      xnor(w0,A[0],B[0]);
10     xnor(w1,A[1],B[1]);
11     xnor(w2,A[2],B[2]);
12     xnor(w3,A[3],B[3]);
13
14     wire [3:0] A_;
15     wire [3:0] B_;
16     not (A_[0],A[0]);
17     not (A_[1],A[1]);
18     not (A_[2],A[2]);
19     not (A_[3],A[3]);
20
21     not (B_[0],B[0]);
22     not (B_[1],B[1]);
23     not (B_[2],B[2]);
24     not (B_[3],B[3]);
25
26
27
28     and(equal,w0,w1,w2,w3);
29
30     and (s0,A[3],B_[3]);
31     and (s1,w3,A[2],B_[2]);
32     and (s2,w2,w3,A[1],B_[1]);
33     and (s3,w1,w2,w3,A[0],B_[0]);
34     or (A_greater,s0,s1,s2,s3);
35
36     and (s4,A_[3],B[3]);
37     and (s5,w3,A_[2],B[2]);
38     and (s6,w2,w3,A_[1],B[1]);
39     and (s7,w1,w2,w3,A_[0],B[0]);
40
41     or (B_greater,s4,s5,s6,s7);
42
43     endmodule
44
```

- The comparison of two numbers is an operation that determines whether one number is greater than, less than, or equal to the other number
- A magnitude comparator is a combinational circuit that compares two

numbers A and B and determines their relative magnitudes

- The outcome of the comparison is specified by three binary variables that indicate whether $A > B$, $A = B$, or $A < B$
- On the one hand, the circuit for comparing two n -bit numbers have 2^{2n} entries in the truth table and becomes too cumbersome, even with $n = 3$
- On the other hand, as one may suspect, a comparator circuit possesses a certain amount of regularity.
- Consider two numbers, A and B, with four digits each $A_3A_2A_1A_0$ and $B_3B_2B_1B_0$
- The two numbers are equal if all pairs of significant digits are equal: $A_3 = B_3$, $A_2 = B_2$, $A_1 = B_1$, and $A_0 = B_0$
- To check bit-wise equality, we can use the XNOR gate
$$x_i = A_i B_i + A_i' B_i' \text{ for } i = 0, 1, 2, 3$$
- For equality to exist, all x_i variables must be equal to 1, a condition that dictates an AND operation of all variables:

$$(A = B) = x_3 x_2 x_1 x_0$$

- To determine whether A is greater or less than B, we inspect the relative magnitudes of pairs of significant digits, starting from the most significant position
- If the two digits of a pair are equal, we compare the next lower significant pair of digits
- The comparison continues until a pair of unequal digits is reached
- If the corresponding digit of A is 1 and that of B is 0, we conclude that $A > B$.

If the corresponding digit of A is 0 and that of B is 1, we have $A < B$

- The comparison can be expressed logically by the two Boolean functions:

$$A > B = A_3 B_3' + x_3 A_2 B_2' + x_3 x_2 A_1 B_1' + x_3 x_2 x_1 A_0 B_0'$$

$$(A < B) = A_3' B_3 + x_3 A_2' B_2 + x_3 x_2 A_1' B_1 + x_3 x_2 x_1 A_0' B_0$$

III) AND BLOCK

```
≡ and.v
1  module And (
2      input [3:0] A,
3      input [3:0] B,
4      output [3:0] out
5  );
6
7  and (out[0],A[0],B[0]);
8  and (out[1],A[1],B[1]);
9  and (out[2],A[2],B[2]);
10 and (out[3],A[3],B[3]);
11
12
13  endmodule
```

IV) ALU

I have also created enabled subcircuits, which send inputs to their corresponding operation block, if the enable is 'High'.

In the ALU testbench, I have created instances of the enable modules, which are responsible for giving the input to the operation modules.

```

tb_alu.v
1  `include "enable_add.v"
2  `include "enable_and.v"
3  `include "enable_comp.v"
4  module tb_alu;
5
6  reg [3:0]A;
7  reg [3:0]B;
8  reg cin, M,e;
9  wire [3:0] sum;
10 wire equal, A_greater, B_greater;
11 wire [3:0] out;
12 wire cout;
13 integer index;
14
15 enable_add F(.A(A),.B(B),.M(M),.cin(cin),.cout(cout),.sum(sum),.e(e));
16 enable_comp dut1(
17     .A(A),
18     .B(B),
19     .equal(equal),
20     .A_greater(A_greater),
21     .B_greater(B_greater),
22     .e(e)
23 );
24
25 enable_and dut(
26     .A(A),
27     .B(B),
28     .e(e),
29     .out(out)
30 );
31
32 initial begin

```

 

2) NgSpice Component

NAND subcircuit used:


```
NAND.sub
1 .subckt NAND node_out node_a node_b vdd gnd
2
3 Mn1 node_out node_a node_y gnd CMOSN W = {wn1} L = {ln1}
4 + AS = {5*wn1*LAMBDA} PS = {10*LAMBDA + 2*wn1} AD = {5*wn1*LAMBDA} PD = {10*LAMBDA + 2*wn1}
5
6 Mn2 node_y node_b gnd gnd CMOSN W = {wn2} L = {ln2}
7 + AS = {5*wn2*LAMBDA} PS = {10*LAMBDA + 2*wn2} AD = {5*wn2*LAMBDA} PD = {10*LAMBDA + 2*wn2}
8
9
10 Mp1 node_out node_a vdd vdd CMOSP W = {wp1} L = {lp1}
11 + AS = {5*wp1*LAMBDA} PS = {10*LAMBDA + 2*wp1} AD = {5*wp1*LAMBDA} PD = {10*LAMBDA + 2*wp1}
12
13 Mp2 node_out node_b vdd vdd CMOSP W = {wp2} L = {lp2}
14 + AS = {5*wp2*LAMBDA} PS = {10*LAMBDA + 2*wp2} AD = {5*wp2*LAMBDA} PD = {10*LAMBDA + 2*wp2}
15
16 .ends NAND
```

I have used this subcircuit to make, AND XOR, XNOR & OR gates.


XOR uses 4 NAND gates.



AND using two NAND gates

 

OR using two NAND gates

 

XNOR using XOR & NAND

Working

The ALU circuit uses full_adder_sub, and_clock , comparator and enable sub-circuit.

Each of the sub-circuit has been implemented according to the logic discussed previously under Verilog.

ALU ckt NgSpice file

```

1  .include TSMC_180nm.txt
2  .include NAND.sub
3  .include OR.sub
4  .include AND.sub
5  .include XOR.sub
6  .include XNOR.sub
7  .include half_adder.sub
8  .include full_adder_sub.sub
9  .include and_block.sub
10
11 .include enable_and_block.sub
12 .include comp.sub
13 .include enable_full_adder_sub.sub
14 .include enable_comp.sub
15
16 .param SUPPLY = 1.8
17 .param LAMBDA = 0.18u
18
19 .param wn1 = {10*LAMBDA}
20 .param wn2 = {10*LAMBDA}
21 .param ln1 = {2*LAMBDA}
22 .param ln2 = {2*LAMBDA}
23
24 .param wp1 = wn1
25 .param wp2 = wn1
26 .param lp1 = {LAMBDA}
27 .param lp2 = {LAMBDA}
28
29 .global gnd
30
31 Vdd node_x gnd 'SUPPLY'
32
33 V_in_a0 a0 gnd PULSE(0 0 0ns 100ps 100ps 20ns 40ns)
34 V_in_a1 a1 gnd PULSE(0 0 0ns 100ps 100ps 50ns 70ns)
35 V_in_a2 a2 gnd PULSE(1.8 1.8 0ns 100ps 100ps 30ns 40ns)
36 V_in_a3 a3 gnd PULSE(1.8 1.8 0ns 100ps 100ps 50ns 100ns)
37
38 V_in_b0 b0 gnd PULSE(1.8 1.8 0ns 100ps 100ps 20ns 40ns)
39 V_in_b1 b1 gnd PULSE(1.8 1.8 0ns 100ps 100ps 50ns 70ns)
40 V_in_b2 b2 gnd PULSE(1.8 1.8 0ns 100ps 100ps 30ns 40ns)
41 V_in_b3 b3 gnd PULSE(0 0 0ns 100ps 100ps 25ns 50ns)
42 V_cin cin gnd PULSE(0 0 0ns 100ps 100ps 50ns 70ns)
43
44
45
46
47
48
49
50
51 X1 A B A_B a0 a1 a2 a3 b0 b1 b2 b3 e1 node_x gnd enable_comp
52 X2 s0 s1 s2 s3 cout M1 a0 a1 a2 a3 b0 b1 b2 b3 cin e2 node_x gnd enable_full_adder_sub
53 X3 s0_ s1_ s2_ s3_ cout_ M2 a0 a1 a2 a3 b0 b1 b2 b3 cin e3 node_x gnd enable_full_adder_sub
54 X4 c0 c1 c2 c3 a0 a1 a2 a3 b0 b1 b2 b3 e4 node_x gnd enable_and_block
55
56 .tran 1n 800n
57
58 .control
59 run
60
61
62 plot V(a0) v(a1)+2 v(a2) +4 v(a3)+6
63 plot v(b0) v(b1)+2 v(b2) +4 v(b3)+6
64 plot v(s0) v(s1)+2 v(s2) +4 v(s3)+6 v(cout) +8
65 plot v(s0_) v(s1_)+2 v(s2_) +4 v(s3_) +6 v(cout_) +8
66 plot v(c0) v(c1)+2 v(c2) +4 v(c3)+6
67 plot v(A) v(B)+2 v(A_B) +4
68
69
70 .end
71 .endc
72
```

3) Magic Component

All the layouts are built using SCN6M_DEEP.09 Cmos technology.

Basic Structure:

- PMOS transistor is formed by placing p-diffusion in an n-well.
- NMOS transistor is formed by placing n-diffusion in a p-well.

Material Usage:

- The gate of both PMOS and NMOS transistors is made using Polysilicon material.
- Polysilicon is connected to metal using polycontact.

Terminology and Connectivity:

- Terminals for the drain and source of PMOS and NMOS are established by connecting metal to the p-diffusion and n-diffusion, respectively.

pdcontact and ndcontact are used to connect metal to p-diffusion and n-diffusion, respectively.

Metal Connectivity:


- Two different metals can overlap, but if they need to be electrically connected, a contact must be placed between them.
- Example: M3contact is used when Metal 3 and Metal 2 need to be connected in the overlapping area.

Specific Constraint:


- Only Metal 1 can be connected directly to polysilicon.

I have made the following gates, which have been used in various sub-circuit layouts.


- 1) 2 INPUT – NAND

 


2) 3 INPUT – NAND

 


3) 4 INPUT NAND

 


4) 5 INPUT NAND

 

5) 2 INPUT NOR

 


6) 4 INPUT OR

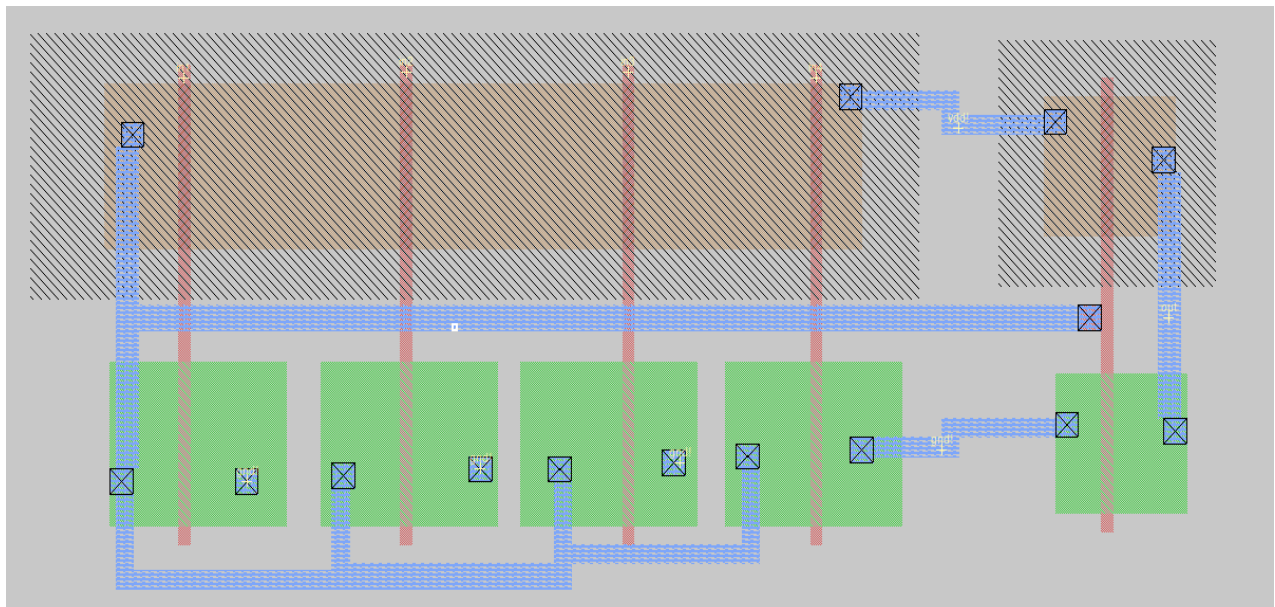


 7) 2 INPUT XOR

**Implemented using 4 two input NAND gates




8) FULL ADDER (series of 4 (3-bit FA's)

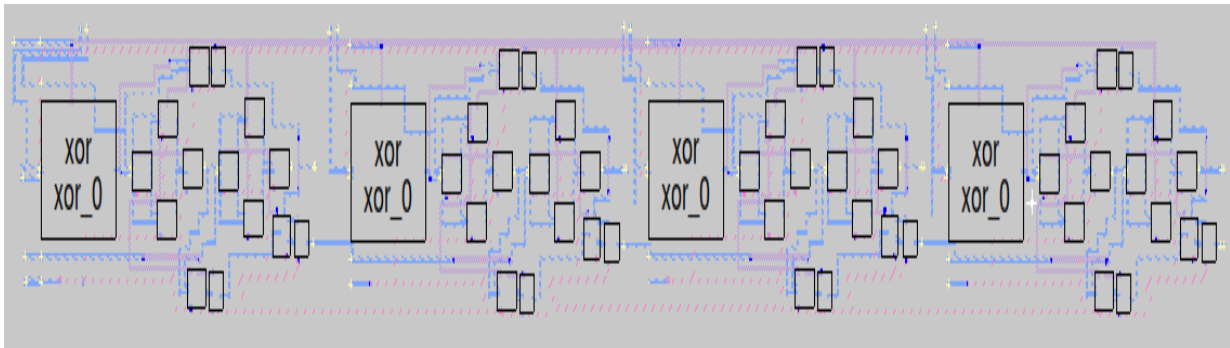

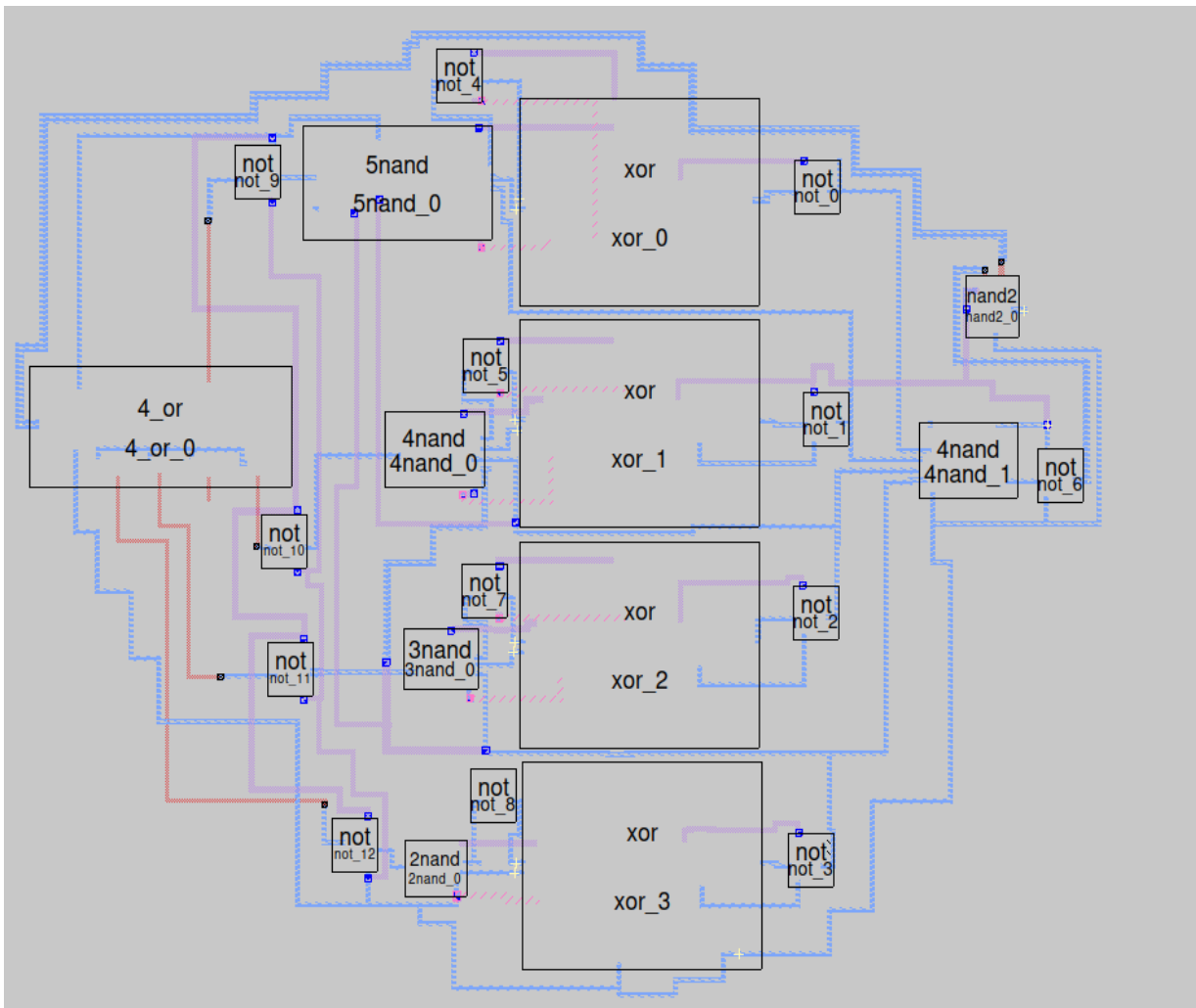
9) COMPARATOR

**Implemented using 5,4,3,2 input NAND gates. Also used XOR and 4 input OR gates.



 10) ALU

This includes the 2:4 decoder, AND block, Comparator and Adder/Subtractor (rotated image)



*DELAY ANALYSIS IS PRESENTED IN A SEPARATE REPORT.

(DELAY ANALYSIS HAS BEEN DONE USING THE EXTRACTED SPICE FILES)